

How to implement multibit shift in hardware?

Let us illustrate the process for a 4-bit number $B = (b_3, b_2, b_1, b_0)$. You can extend the idea for 8-bit or 32-bit numbers in the future.

a) Consider logical right shift


Shift by 0: $B = (b_3, b_2, b_1, b_0) \rightarrow B_0 = (b_3, b_2, b_1, b_0)$

Shift by 1: $B = (b_3, b_2, b_1, b_0) \rightarrow B_1 = (0, b_3, b_2, b_1)$

Shift by 2: $B = (b_3, b_2, b_1, b_0) \rightarrow B_2 = (0, 0, b_3, b_2)$

Shift by 3: $B = (b_3, b_2, b_1, b_0) \rightarrow B_3 = (0, 0, 0, b_3)$

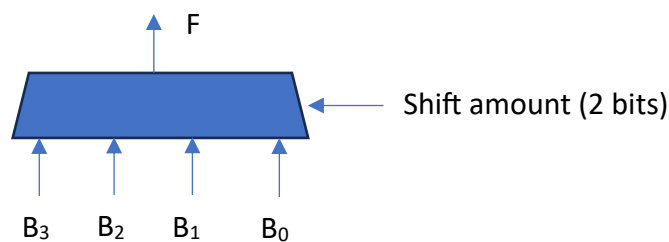Consider a multiplexer circuit as shown below.



Actually, there are four 4-to-1 multiplexers. To generate B_0 , B_1 , B_2 and B_3 , you do not need any extra circuits; just some wiring. This circuit can generate shifted data by any desired amount.

b) Consider arithmetic right shift

Shift by 0: $B = (b_3, b_2, b_1, b_0) \rightarrow B_0 = (b_3, b_2, b_1, b_0)$

Shift by 1: $B = (b_3, b_2, b_1, b_0) \rightarrow B_1 = (b_3, b_3, b_2, b_1)$

Shift by 2: $B = (b_3, b_2, b_1, b_0) \rightarrow B_2 = (b_3, b_3, b_3, b_2)$

Shift by 3: $B = (b_3, b_2, b_1, b_0) \rightarrow B_3 = (b_3, b_3, b_3, b_3)$

This can again be implemented using multiplexers.

c) Consider shift left

Shift by 0: $B = (b_3, b_2, b_1, b_0) \rightarrow B_0 = (b_3, b_2, b_1, b_0)$

Shift by 1: $B = (b_3, b_2, b_1, b_0) \rightarrow B_1 = (b_2, b_1, b_0, 0)$

Shift by 2: $B = (b_3, b_2, b_1, b_0) \rightarrow B_2 = (b_1, b_0, 0, 0)$

Shift by 3: $B = (b_3, b_2, b_1, b_0) \rightarrow B_3 = (b_0, 0, 0, 0)$

This can again be implemented using multiplexers.

For 8-bit data, you will need eight 8-to-1 multiplexers. For 32-bit data, you will need 32 32-to-1 multiplexers.

How to count number of 1's in an 8-bit data word?

Let the data word be denoted as $B = (b_7, b_6, b_5, b_4, b_3, b_2, b_1, b_0)$. We have to add all the bits of the number using a combinational circuit. We are not allowed to use a shift register or a counter with multiple clock pulses to do this.

We can do this using a tree of adders of progressively larger sizes – 1-bit adder (same as a full adder, can add three bits), 2-bit adder, and 3-bit adder. One possible schematic is shown below.

